

Whammy 4 – NEO – Version 1.11
By melatroid

Working Final Version




melatroid@gmail.com

Note.:


The LM2596HV used in previous versions is not good, as it causes problems when closing the housing. The new bridge rectifier can be built yourself using diodes or used as a ready-made component.



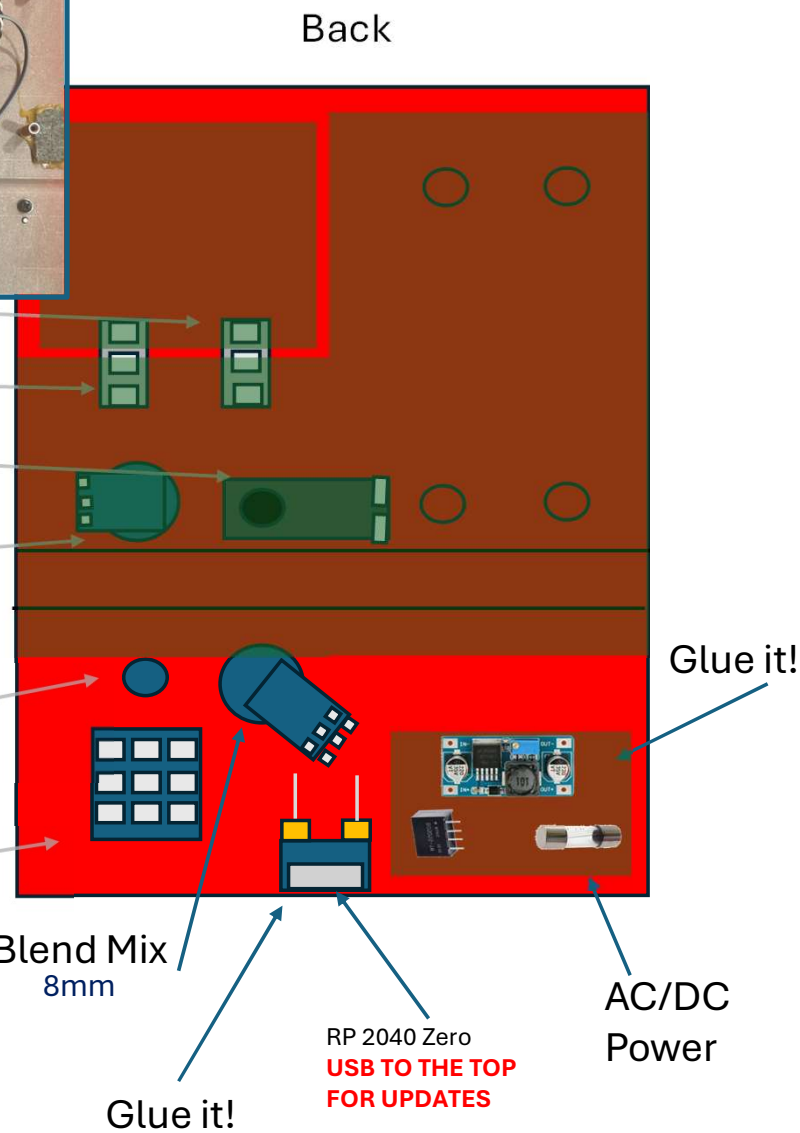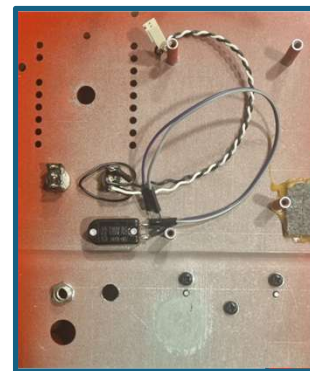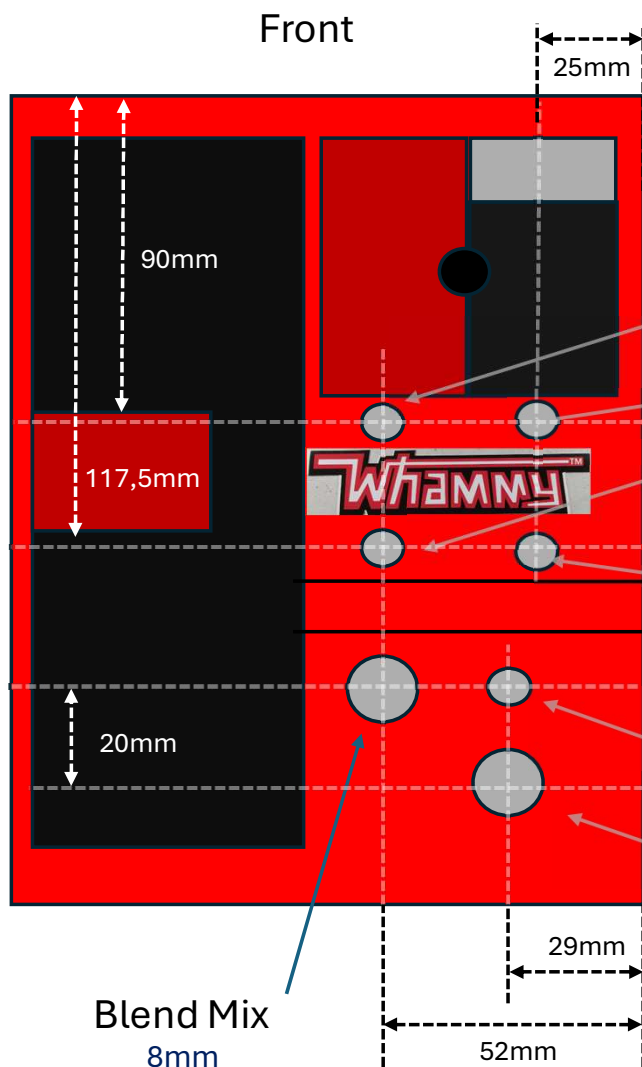- Calibration
- Midi Access
- Time
- Momantary / Change Effects
- Blend Mix
- LED On/OFF
- Effect On/OFF



Parts

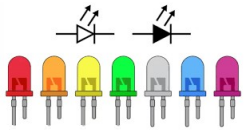

1N4001 4x



1 - 1,2kΩ 1x



220Ω 2x



22-47
uF



100 nF
47 nF

ELKO/Ceramic
Condensers

Fuse (lazy)

250-315 mA



Toogle Switch 2x
Midi Access /
Calibration



Momantary
(Original Part)



250kΩ
Blend



3PDT


B0505S-1W



DC/DC
LM2596



10KΩ

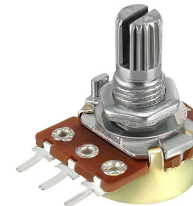




Raspberry Pi
2040 Zero




any small circuit board,
i use this ->

**ElectroCookie Snappable
PCB**

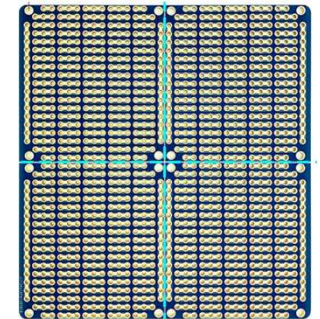

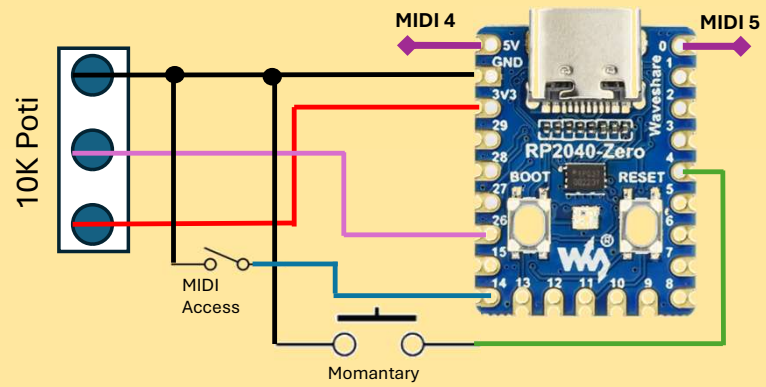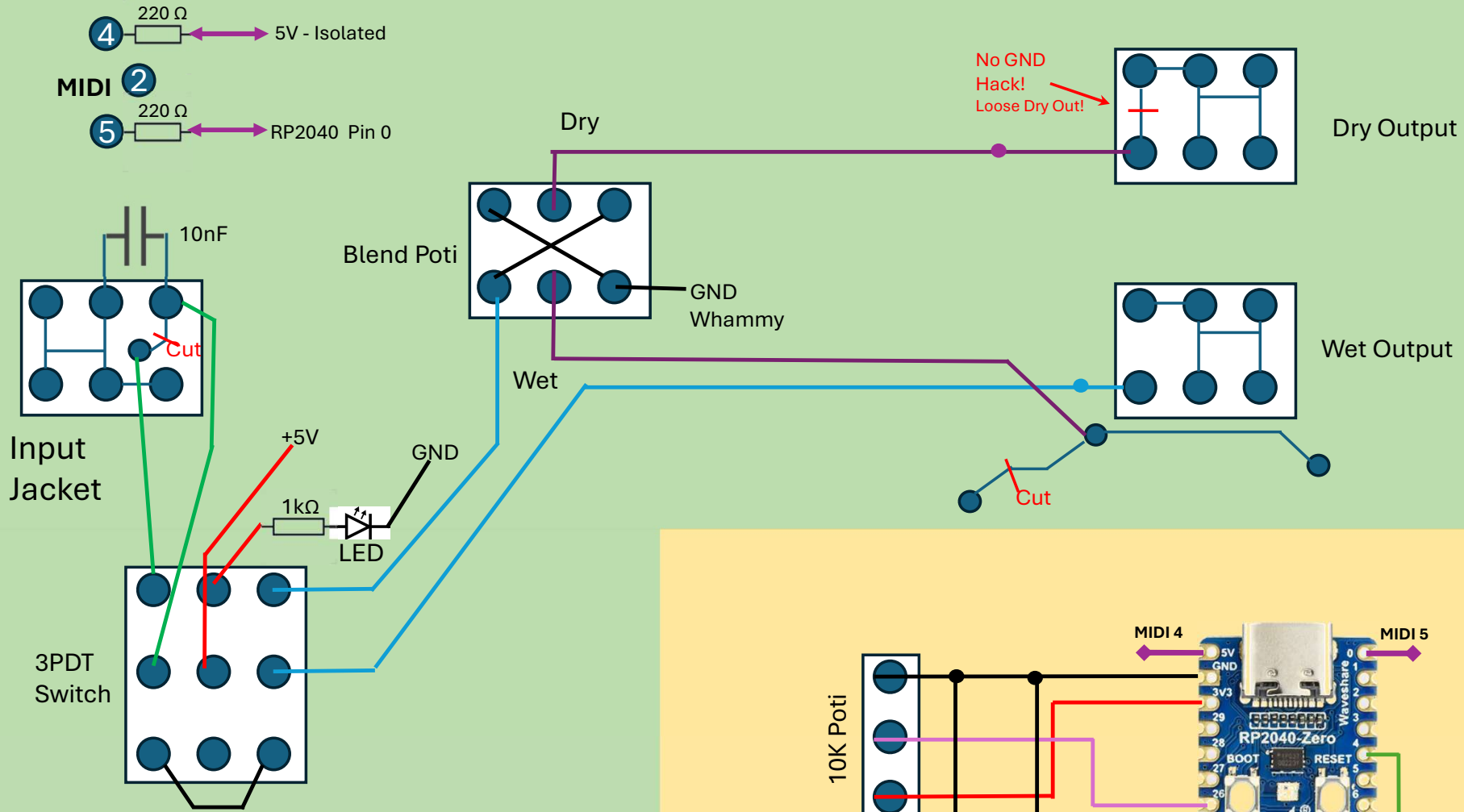


Power Supply

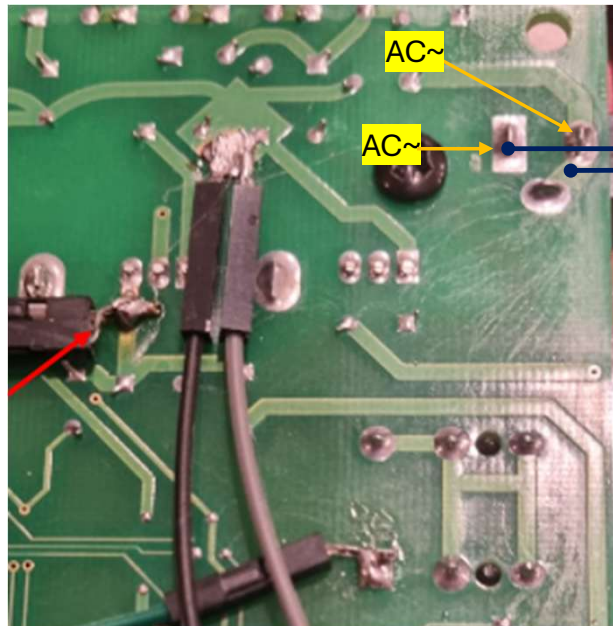

USE REPLACEMENT!!!
NEXT PAGE


~9V

Dont connect to
Source DC GND!!!
Separat DC !

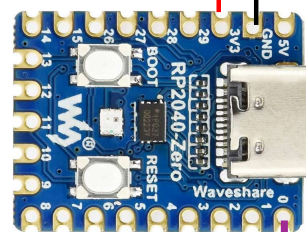


MIDI 5

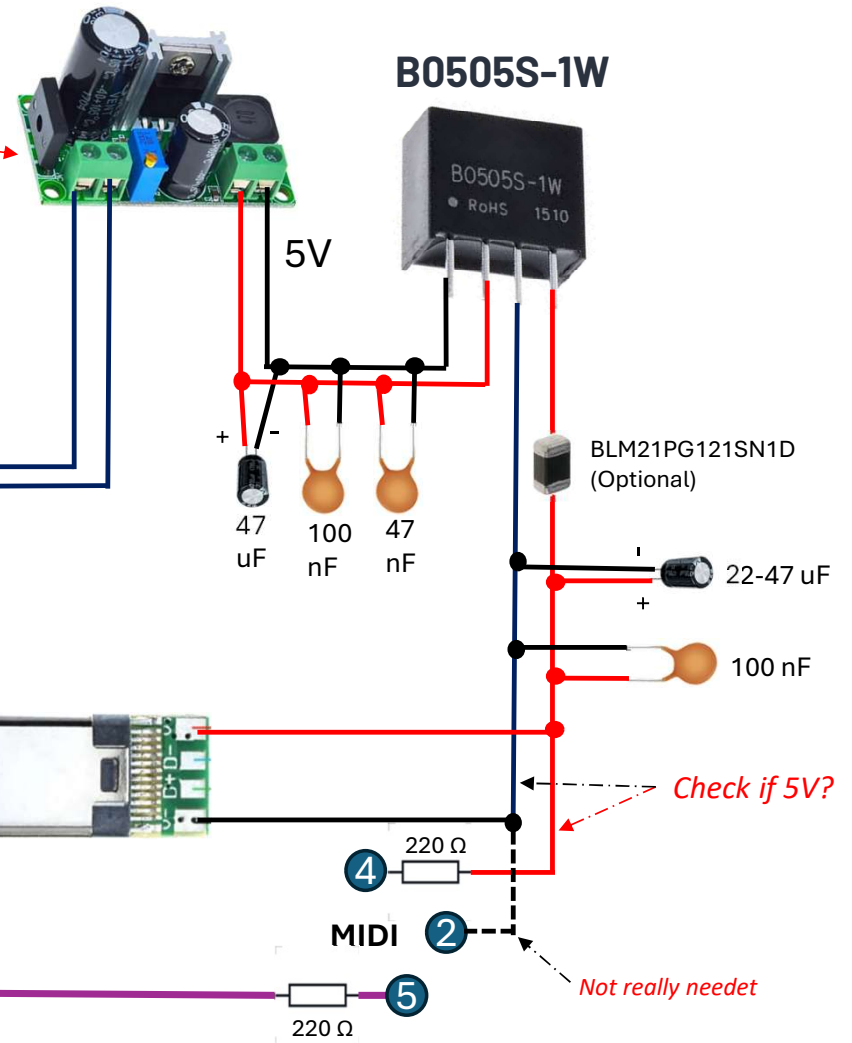Dont connect 2040 Zero
bevor Voltage is correct!




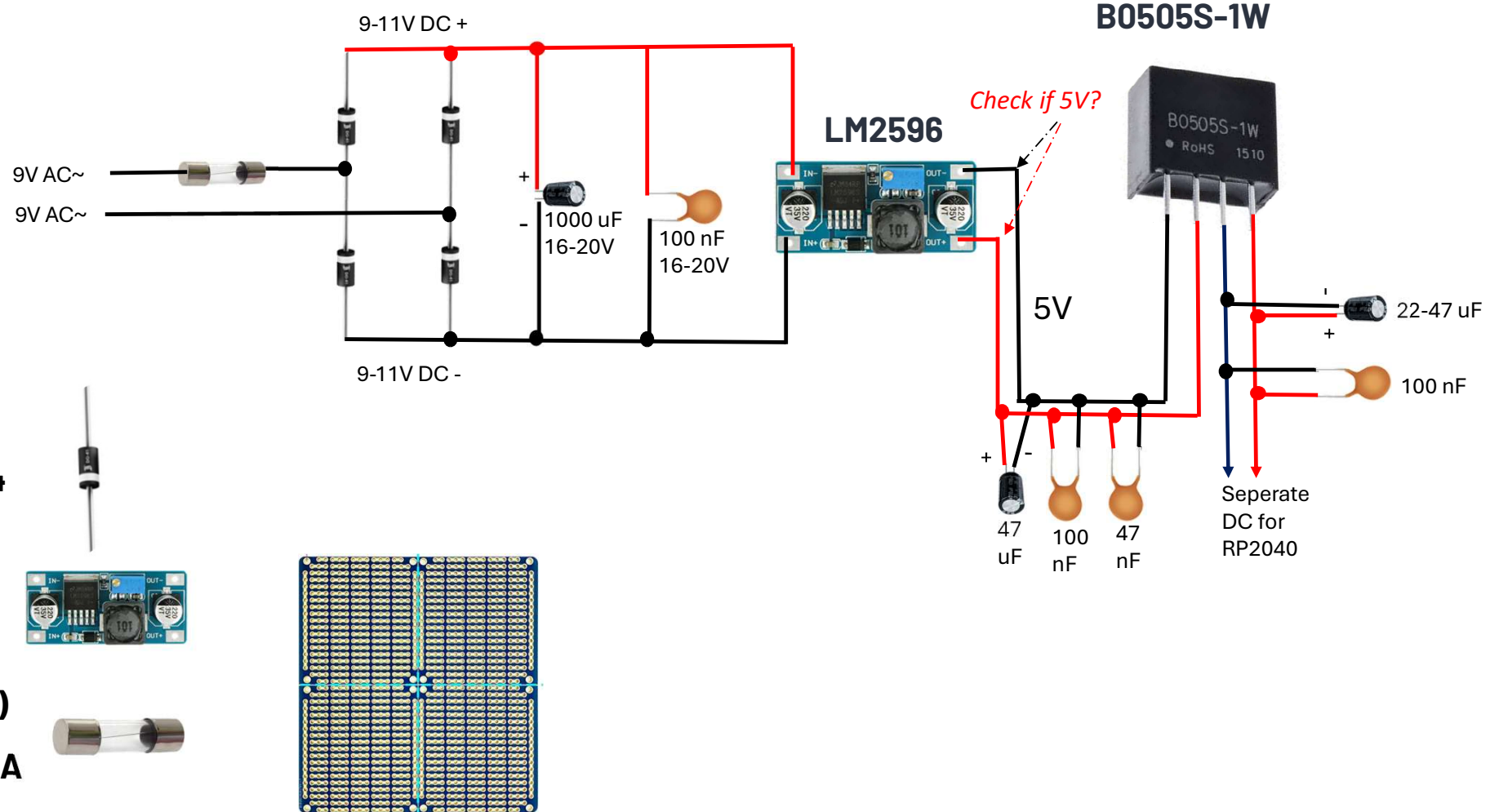Power Supply Replacement (Best) for LM2596HV







Power Supply **PLAN C**



MT3605 OR TPS61023

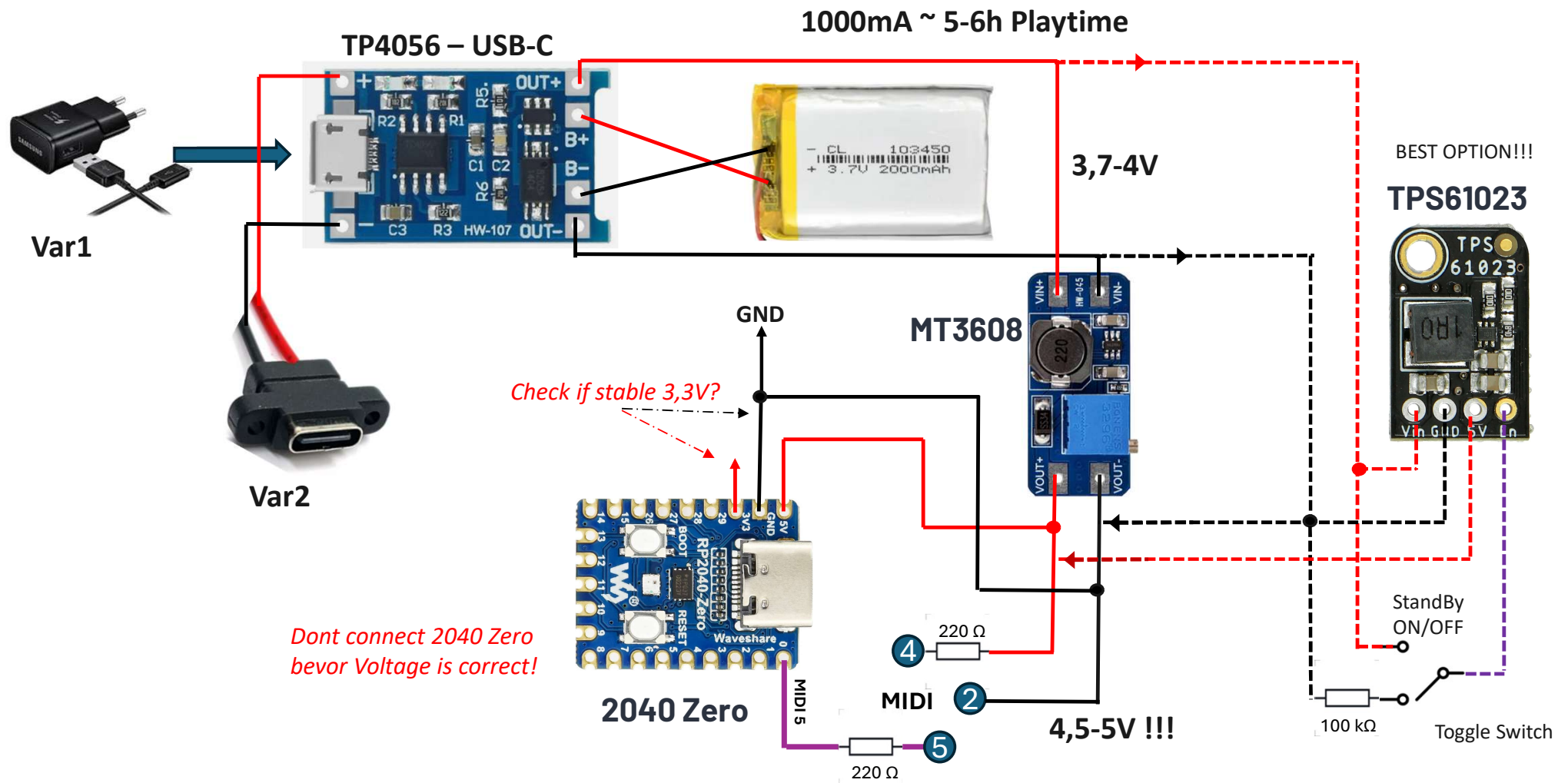

Power Supply Test

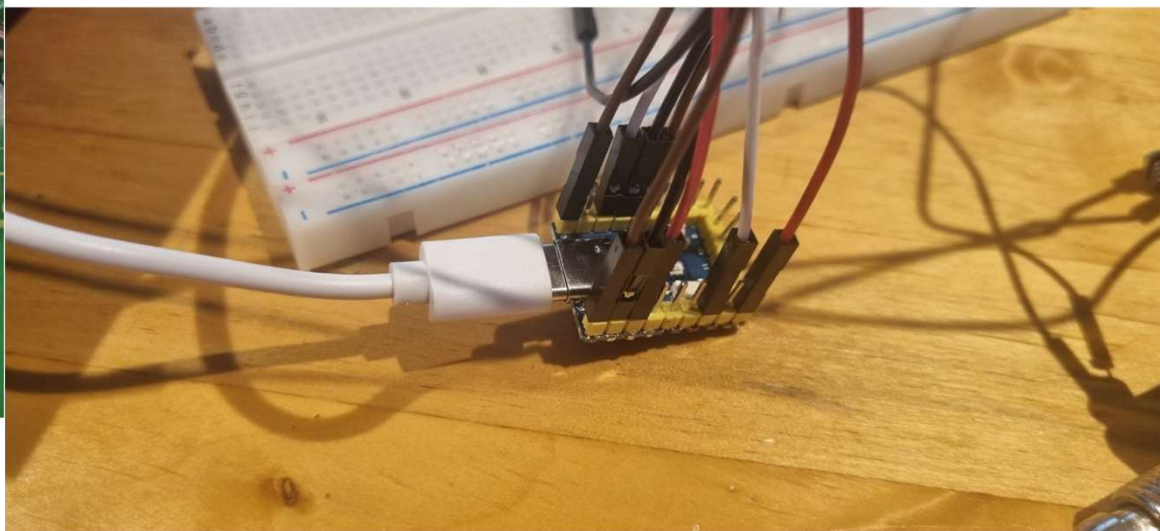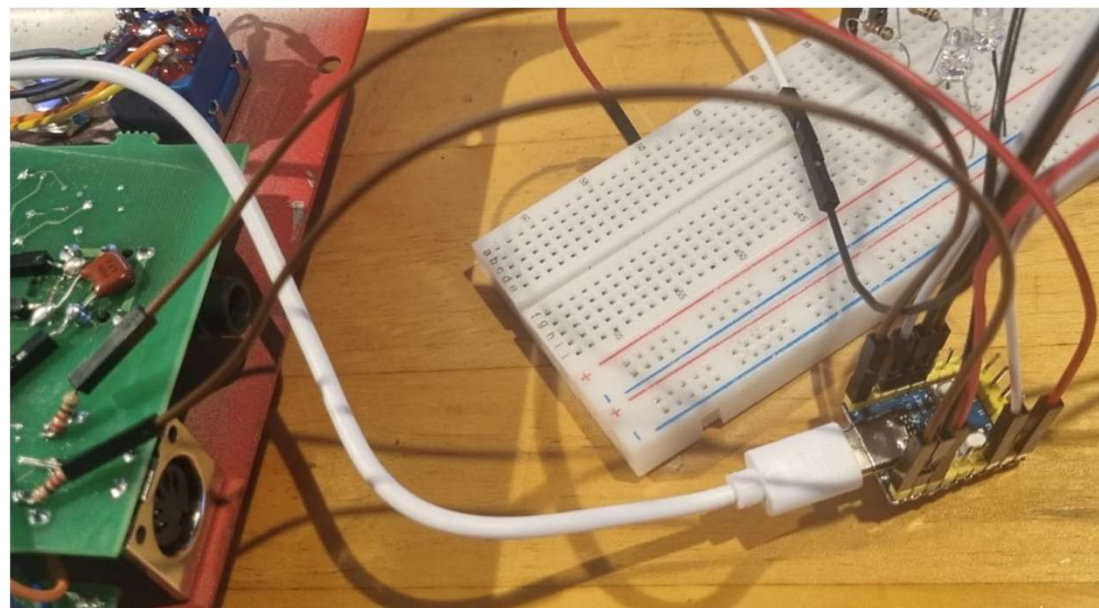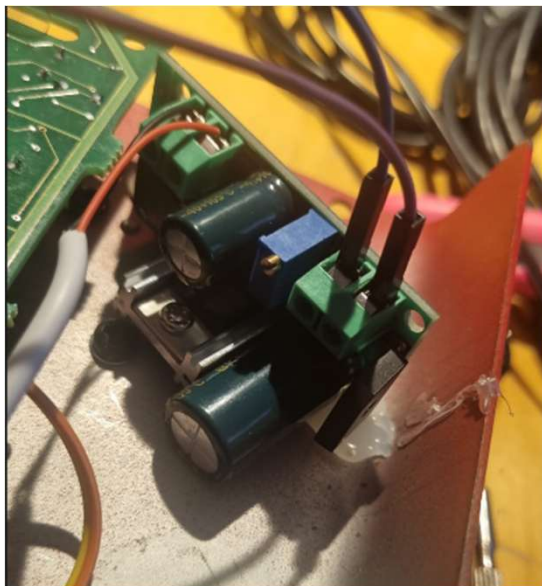



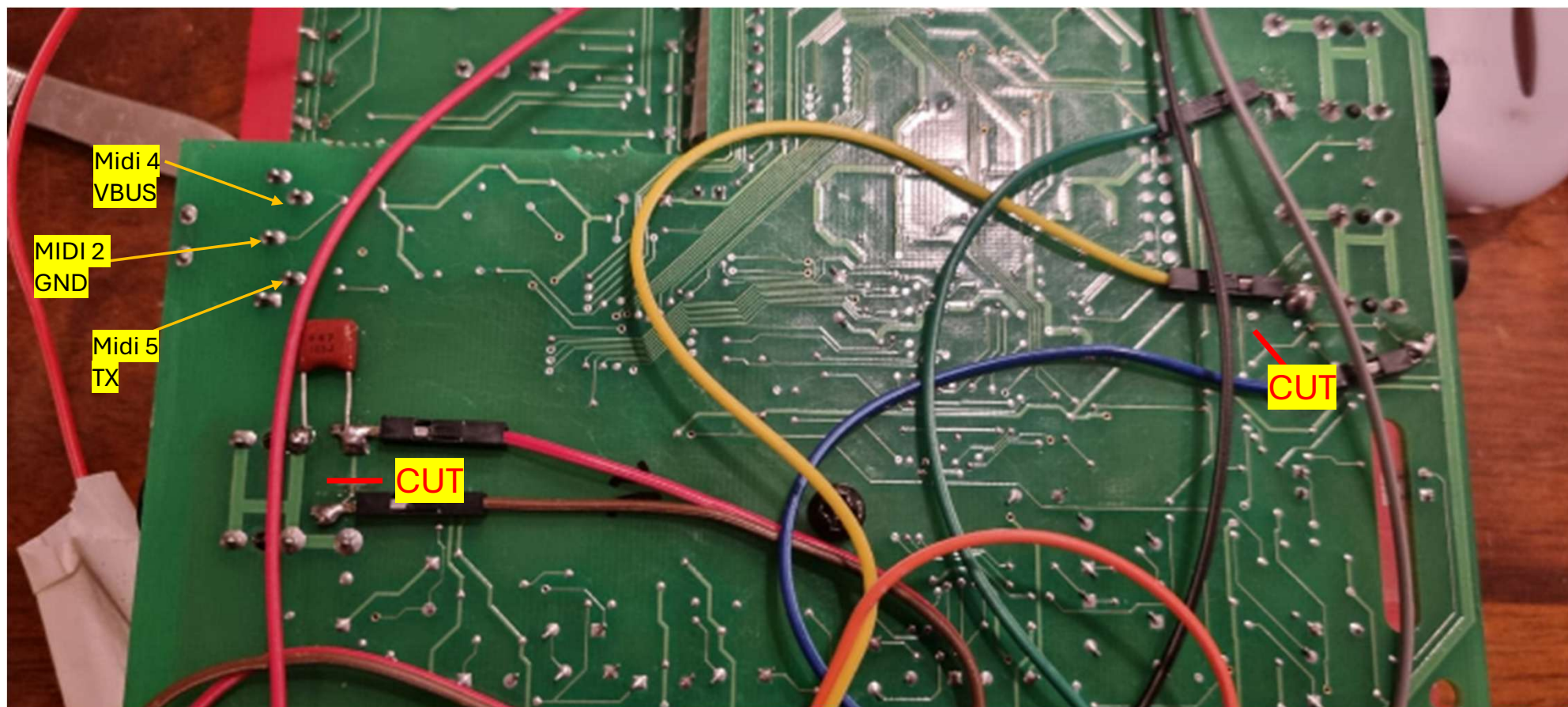


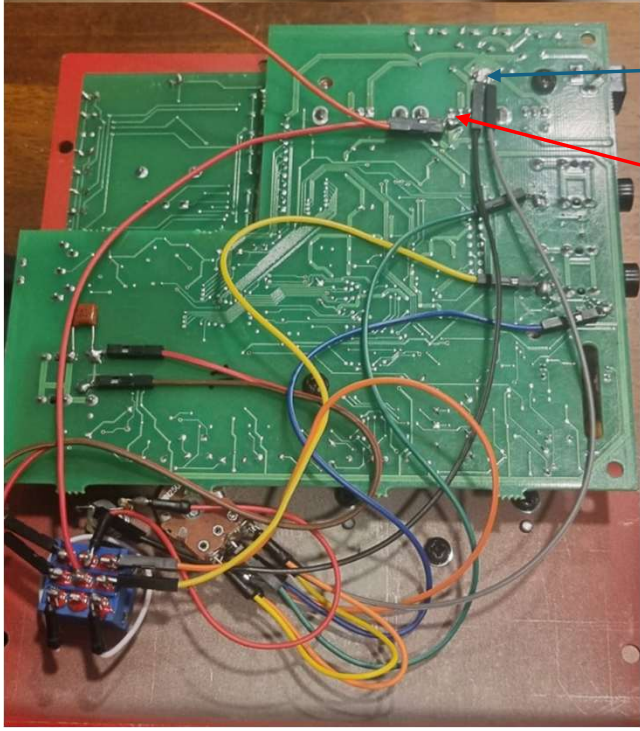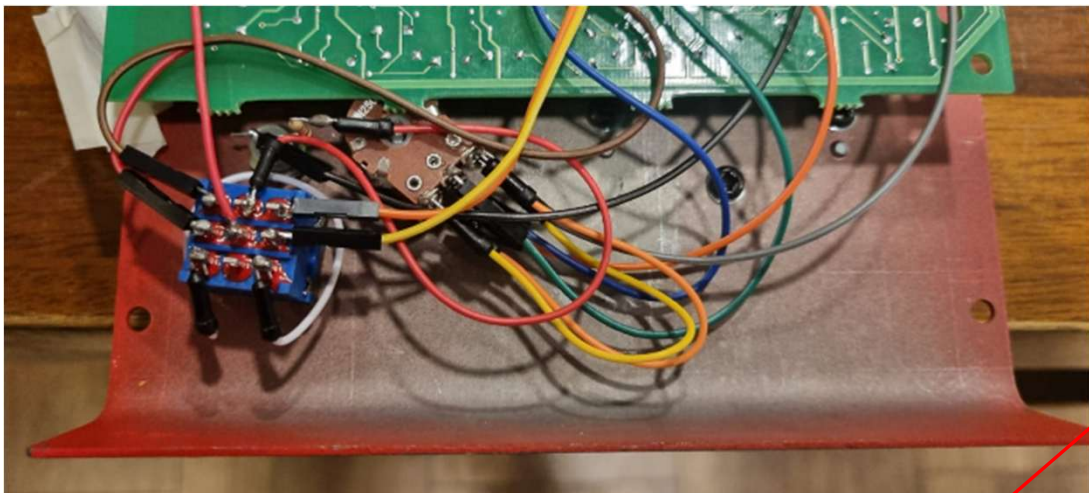




GND LED
HERE!!!

+5V LED
HERE!!!

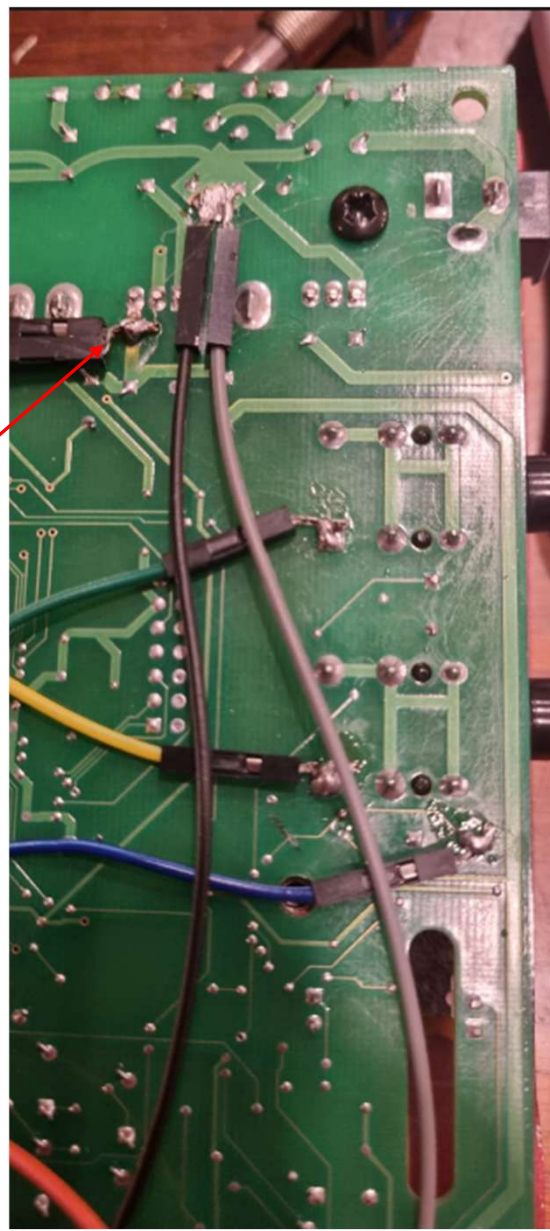

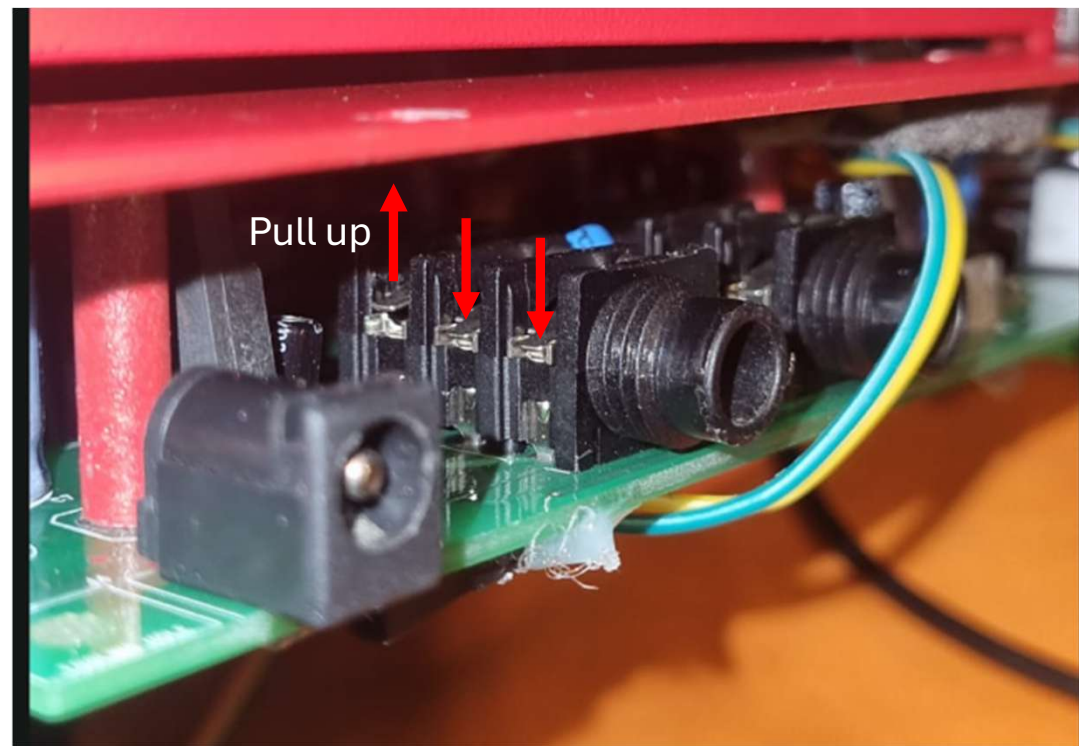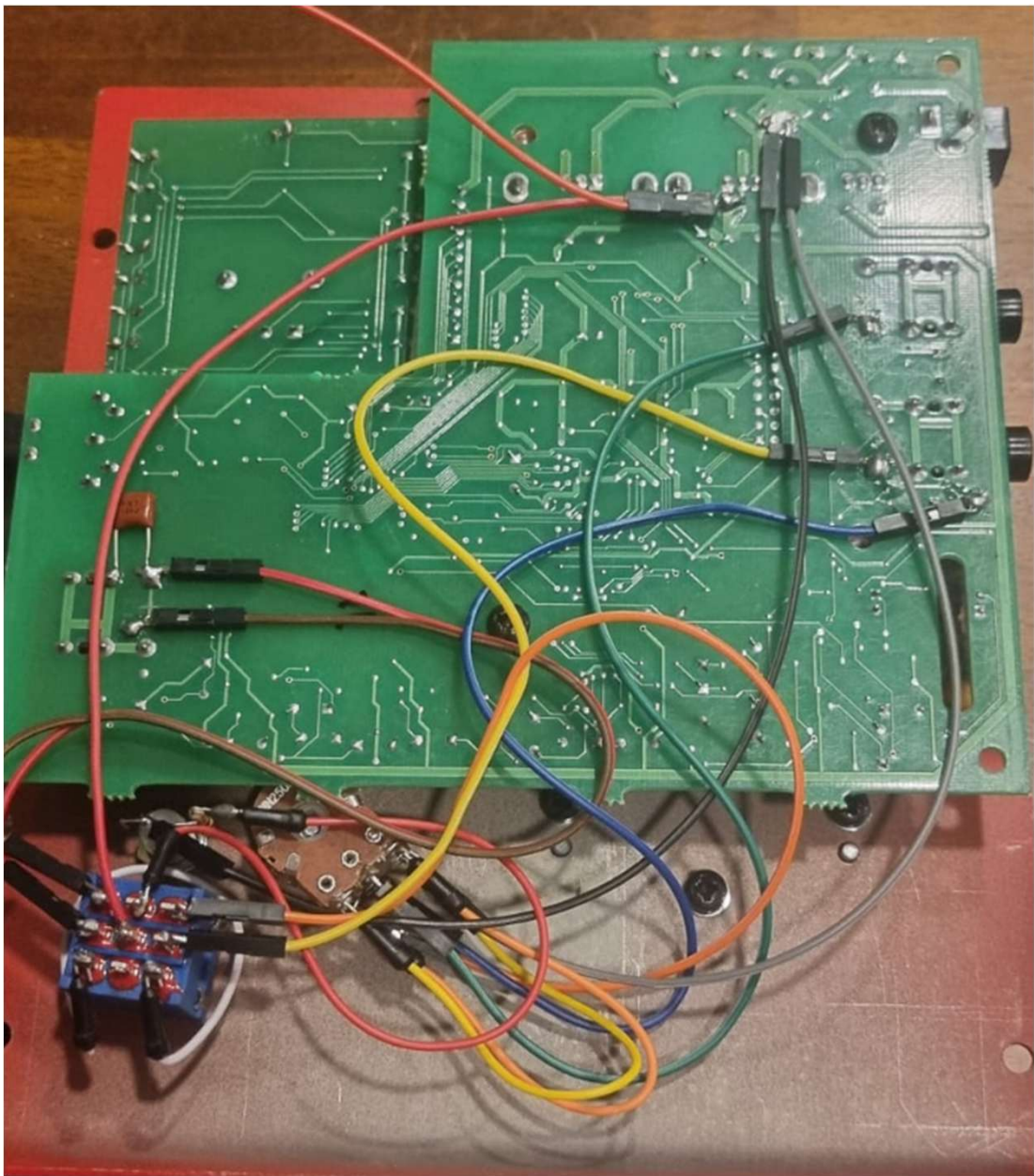




Midi Test

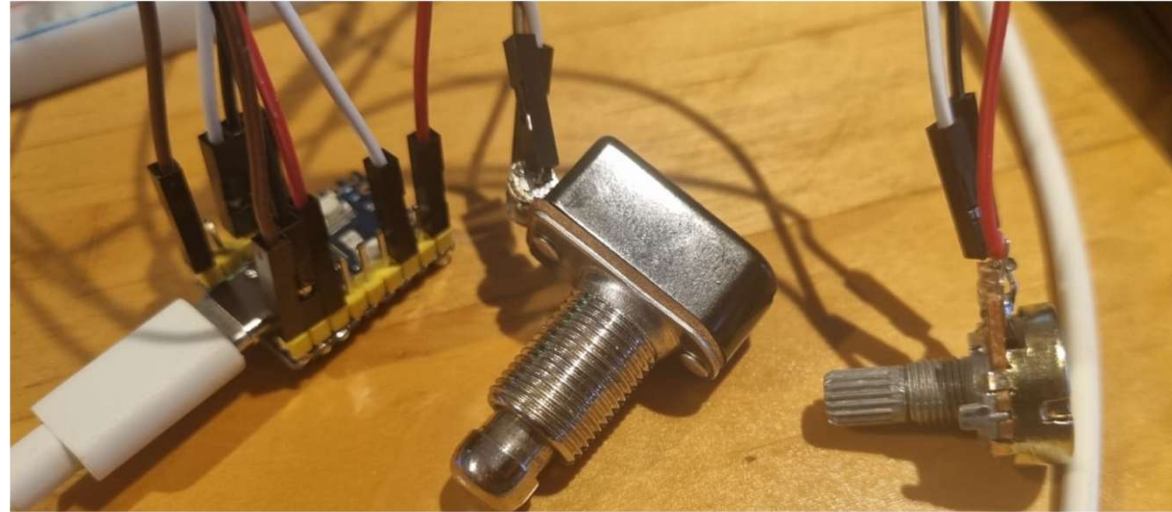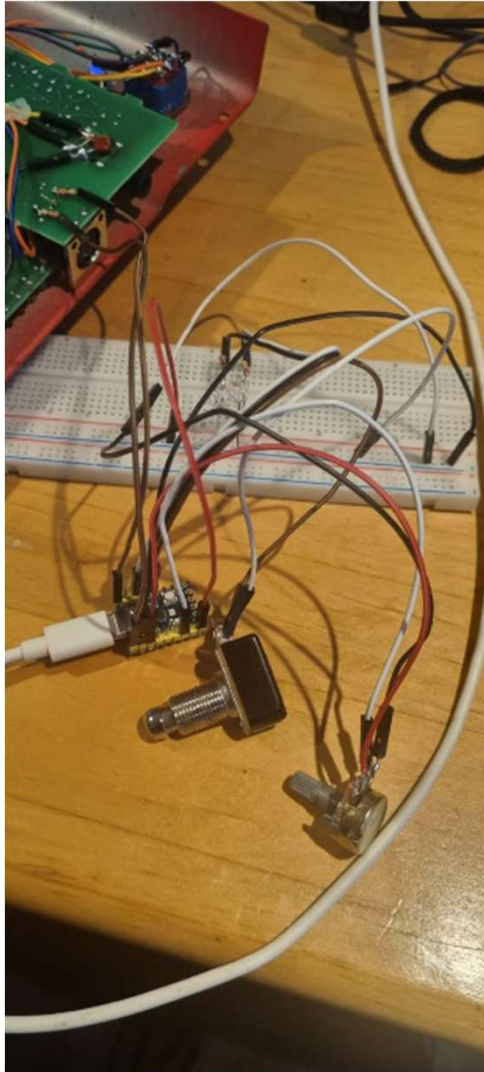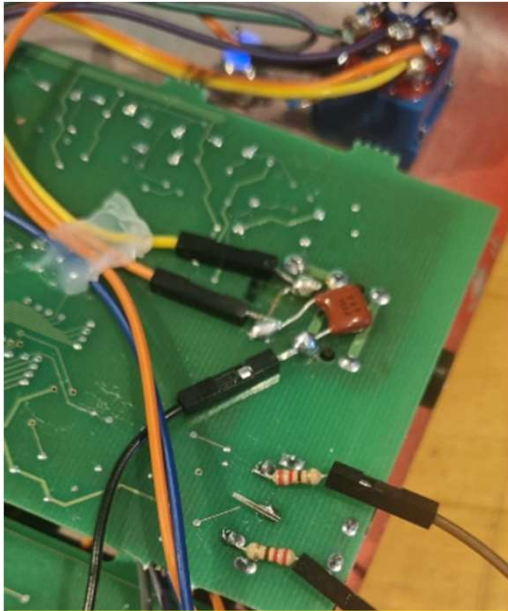


<https://youtube.com/shorts/wjgEext1rCg>

- 2 combinable effect presets

Anti- Noise-Filter

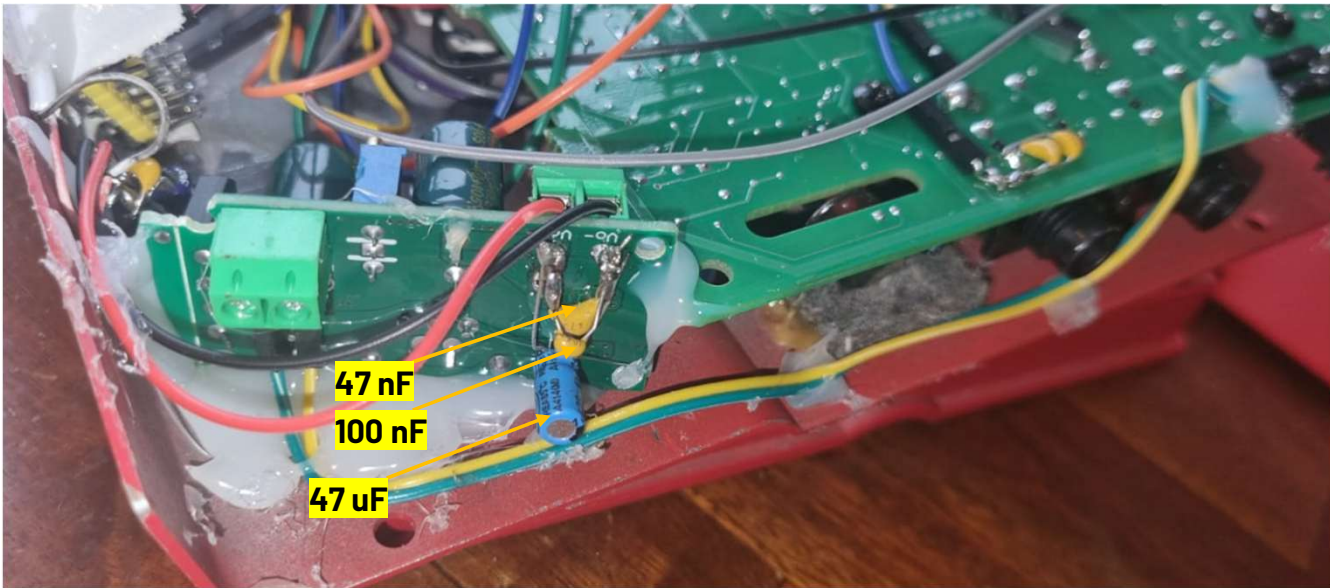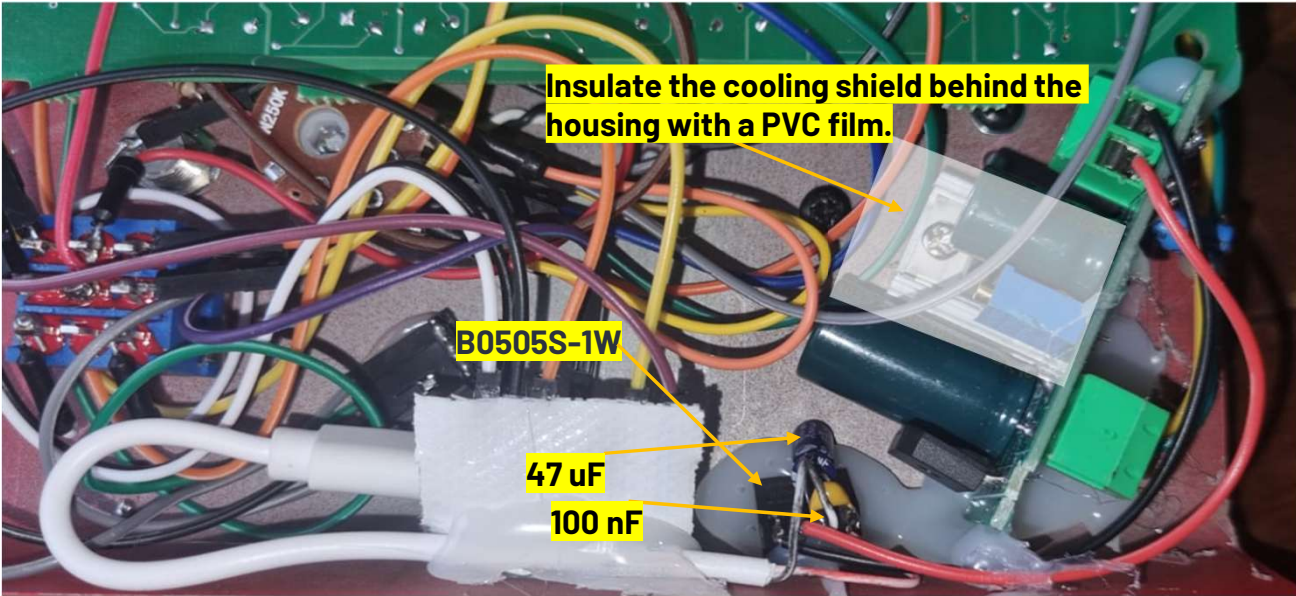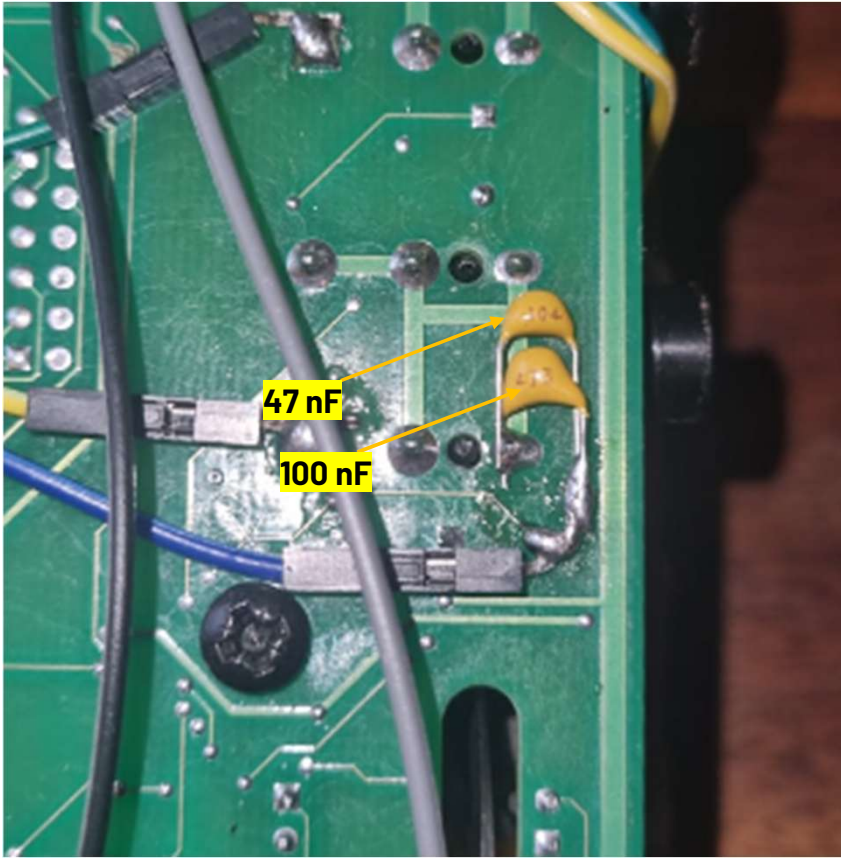

Final Front/Back

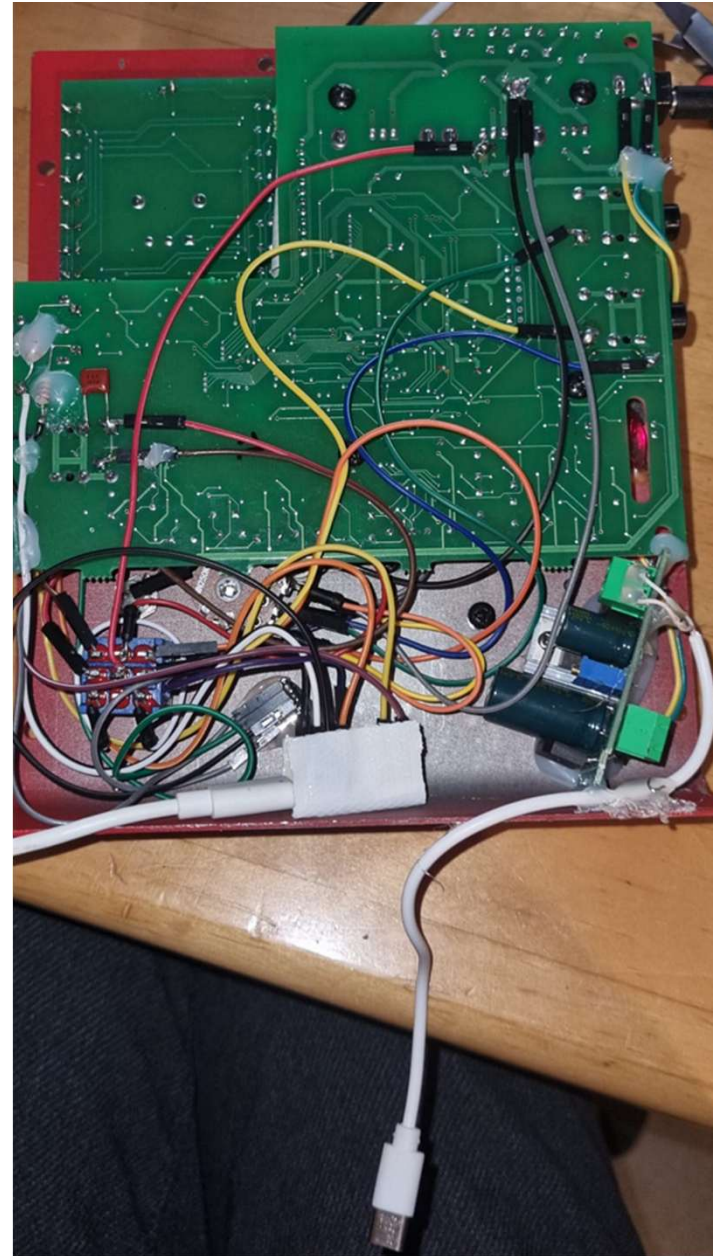

**Flash NEO
Software**

